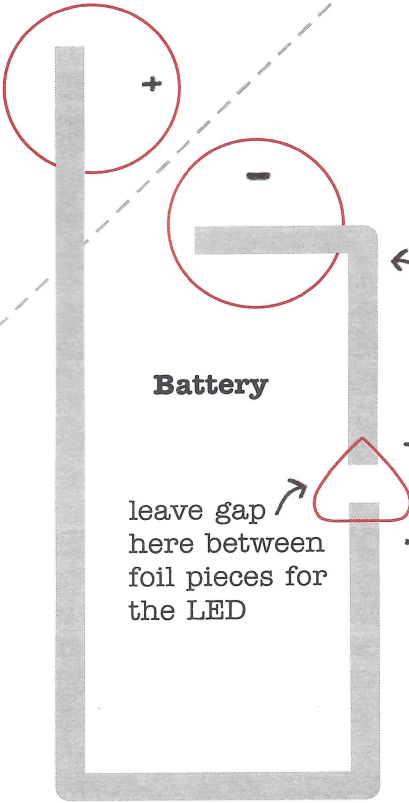


### SIMPLE CIRCUIT TEMPLATE



use one continuous strip of foil

**Battery**


leave gap here between foil pieces for the LED

**LED**

tape down the foil first and place the LED on top

use another continuous strip of foil

### SIMPLE CIRCUIT TEMPLATE

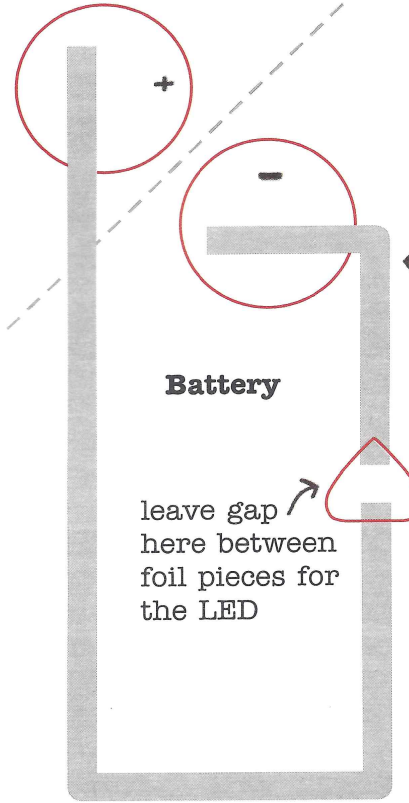

use one continuous strip of foil

**Battery**


leave gap here between foil pieces for the LED

**LED**

tape down the foil first and place the LED on top

use another continuous strip of foil

### SIMPLE CIRCUIT TEMPLATE

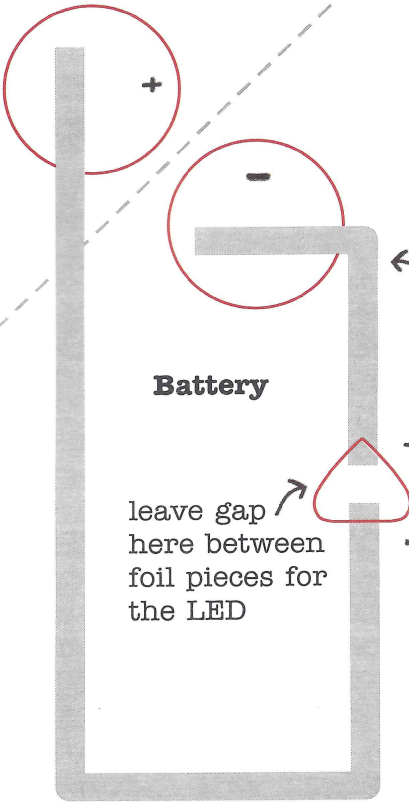

use one continuous strip of foil

**Battery**


leave gap here between foil pieces for the LED

**LED**

tape down the foil first and place the LED on top

use another continuous strip of foil

### SIMPLE CIRCUIT TEMPLATE

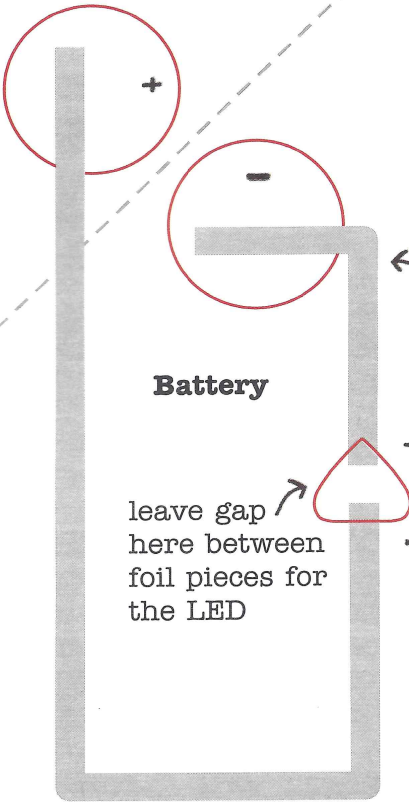

use one continuous strip of foil

**Battery**

leave gap here between foil pieces for the LED

**LED**

tape down the foil first and place the LED on top

use another continuous strip of foil

